

Test Examination 2014
Department of Computer Science
Part-I Honours
Bangabasi College

Time 4Hrs

Full Marks:100

Answer Q.No 1 and Any Six from rest.

Short Question (Answer any *Eleven*)

11x2=22

1.
 - a) Can the barrier potential of a junction diode be measured by a Voltmeter? Explain
 - b) Distinguish between Zener breakdown and avalanche breakdown.
 - c) What is the PIV in rectification?
 - d) Define the Cut-in voltage of a p-n diode. What are its typical values for Ge and Si diodes?
 - e) What is radix of a number system? state with examples.
 - f) Add: $(1.350)_6 + (24)_6$.
 - g) Subtract: $01100 - 00011$ using 2's complement method.
 - h) Proof that $X(Y+Z) = XY+XZ$.
 - i) What is glitch?
 - j) What is stored memory architecture?
 - k) What is the difference between ROM and PROM?
 - l) What is cache memory?
 - m) What is virtual memory?
 - n) State difference between Compiler and Assembler?
 - o) Compare between System Software and Application Software.
 - p) State the purpose of any four symbols used in a flowchart.
 - q) What do you understand by an integer variable?

2.
 - a) State De-Morgan's Law.
 - b) Compare and contrast at least three bus structures.
 - c) What are the advantages of having floating point arithmetic with unnormalized form?
 - d) Design a combinational circuit with four lines as inputs and whose output complement of the input number.
 - e) What do you mean by Multiprocessing. 2+3=3+4 1

3.
 - a) Show that dual of the exclusive OR is equal to its complement. Prove or disprove Whether it is equally true for the exclusive NOR
 - b) What is translator? Give two examples.
 - c) Discuss about the evolution of computer system since 1940s? 4+3+6

4.
 - a) What is Zener diode?
 - b) In Zener diode voltage regulator circuit, the source series resistance $R_s = 20 \text{ Ohm}$. Zener voltage $V_z = 18 \text{ volt}$ and load resistance $R_L = 200 \text{ Ohm}$. If source voltage can Vary from 20 volt to 30 volt, find max and min current in the diode.

- c) What do you mean by the Junction Capacitance of p-n diode? Does it depend the depletion layer width and the applied reverse bias.
- d) Define static and dynamic resistance of p-n diode

5. a) Implement the function with only AND & NOT Gates

$$F = xy + x'y' + y'z$$

- b) Why filter is used in rectification?
- c) For a Half-wave and full-wave rectifier, calculate
 - i) Form Factor.
 - ii) Ripple Factor.
 - iii) Efficiency of rectification.

$$5+2+(3 \times 2) = 13$$

6. a) Explain the operation of JK ff.
 b) What is race around condition? How this race problem can be overcome by using JK master-slave ff?
 c) What is T ff? Mention its use.
 d) Convert a SR ff to JK ff. Show the details design.

$$3+(2 \times 2) = 7$$

7. a) A combinational circuit is specified by the following three Boolean functions.

$$F_1(A,B,C) = \Sigma(3,5,6)$$

$$F_2(A,B,C) = \Sigma(1,4)$$

$$F_3(A,B,C) = \Sigma(2,3,5,6,7)$$

Implement the circuit with a decoder constructed with NAND gates and NAND or AND gates connected to the decoder output.

- b) Realize $F(A,B,C,D) = \Sigma(0,1,3,5,6,8,9,13,15)$ using 8x1 Mux
- c) Design a BCD to Gray code Converter using Mux.

$$4 + 4 + 5 = 13$$

8. Given a linked list whose nodes contain numeric data values. Write algorithms to :-

- a) Compute sum of the data values.
- b) Return the maximum of data values.
- c) Count the number of nodes.

$$5+4+4$$

9. a) What is recursion? Explain with any recursive function of your choice.

- b) With respect to a singly linked list, write the following algorithms:-
 - i) Create the linked list.
 - ii) Search for a given node whose key value is input from user.

$$4+4+5$$

10. With respect to a singly linked list, write algorithms for functions to

- a) Insert an element at the beginning of the list.
- b) Insert an element before a given node.
- c) Delete an element.

Also include algorithm for any other user defined function incorporated